

TFE4188 - Introduction to Lecture 2

ICs and ESD

Goal

Understand the **real-world** constraints on our IC

Understand why you must **always handle ESD** on an IC

RRPLY

The project for 2023 is to design an integrated temperature sensor.
The hope is that some will tapeout on the Google/Efabless Open
MPW shuttle

The real world constrains our IC


Q: What blocks must our IC include?

E S D

Electrostatic Discharge

If you make an IC, you must consider Electrostatic Discharge (ESD) Protection circuits

Standards for testing at [JEDEC](#)

 

ESD in Silicon Integrated Circuits

Second Edition

AJITH AMERASEKERA | CHARVAKA DUVVURY

When do ESD events occur?

Before/during PCB

Human body model (HBM)

**Charged device model
(CDM)**


After PCB

Human body model (HBM)

System level ESD


Human body model (HBM)

 - Models a person touching a device with a finger
- **Long** duration (around 100 ns)
- Acts like a current source into a pin
- Can usually be handled in the I/O ring
- 4 kV HBM ESD is 2.67 A peak current




An ESD zap example

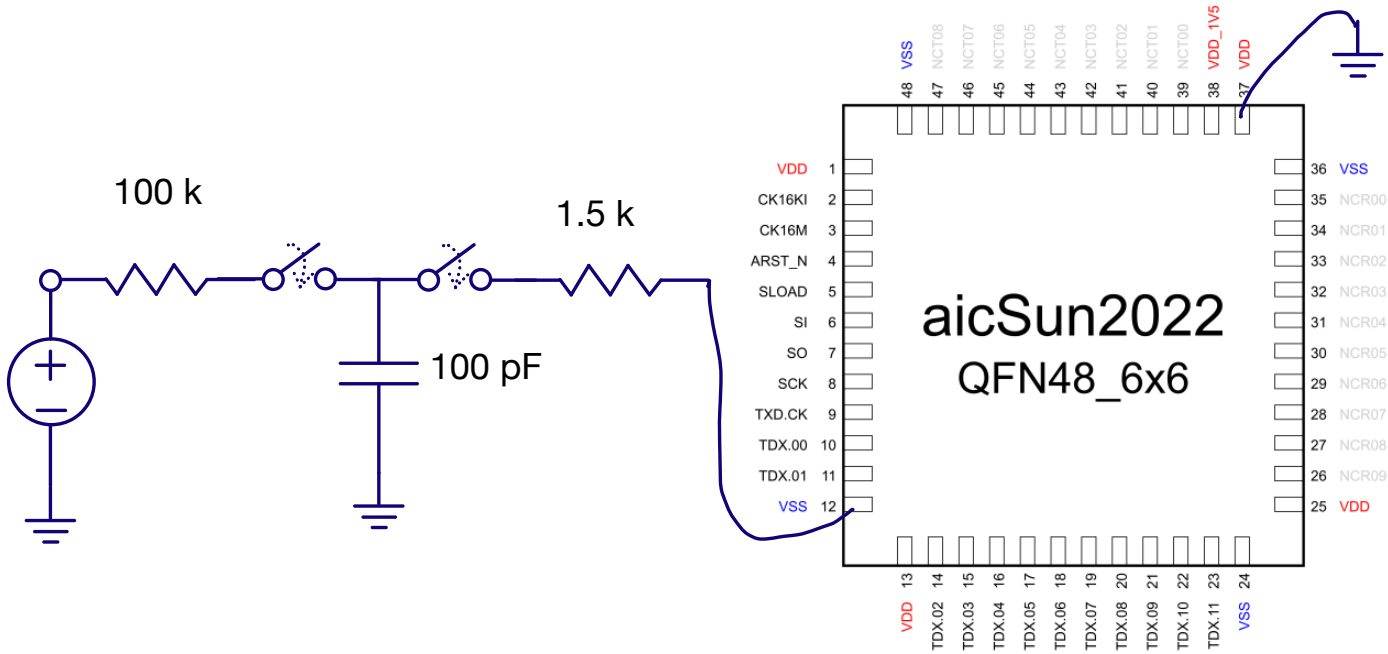
Imagine a ESD zap between VSS and VDD. How can we protect the device?




Permutations

 
0 → 1 VSS → VDD
1 → 0 VDD → VSS
0 → 2 VSS → PIN
2 → 0 PIN → VSS
1 → 2 VDD → PIN
2 → 1 PIN → VDD




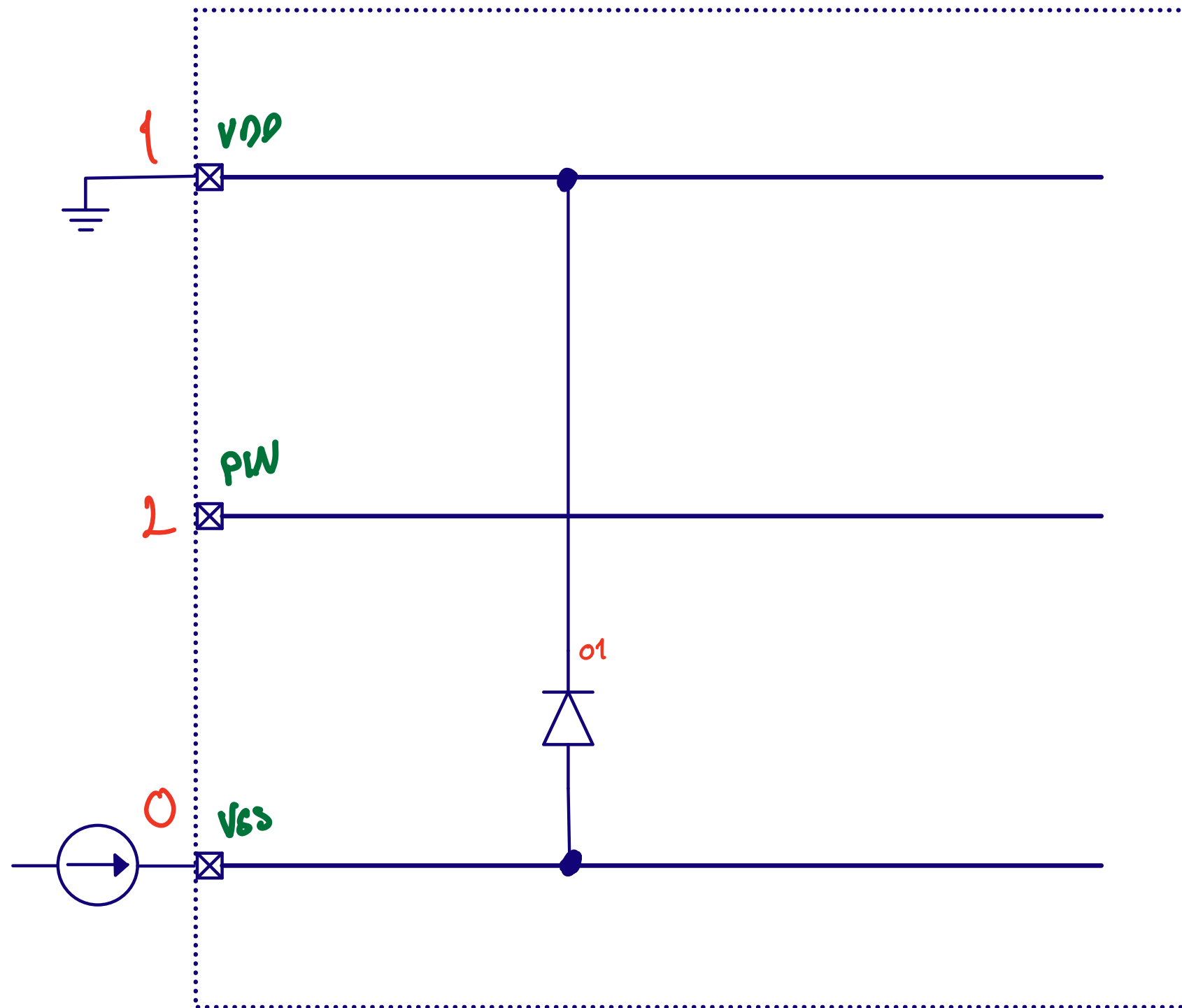

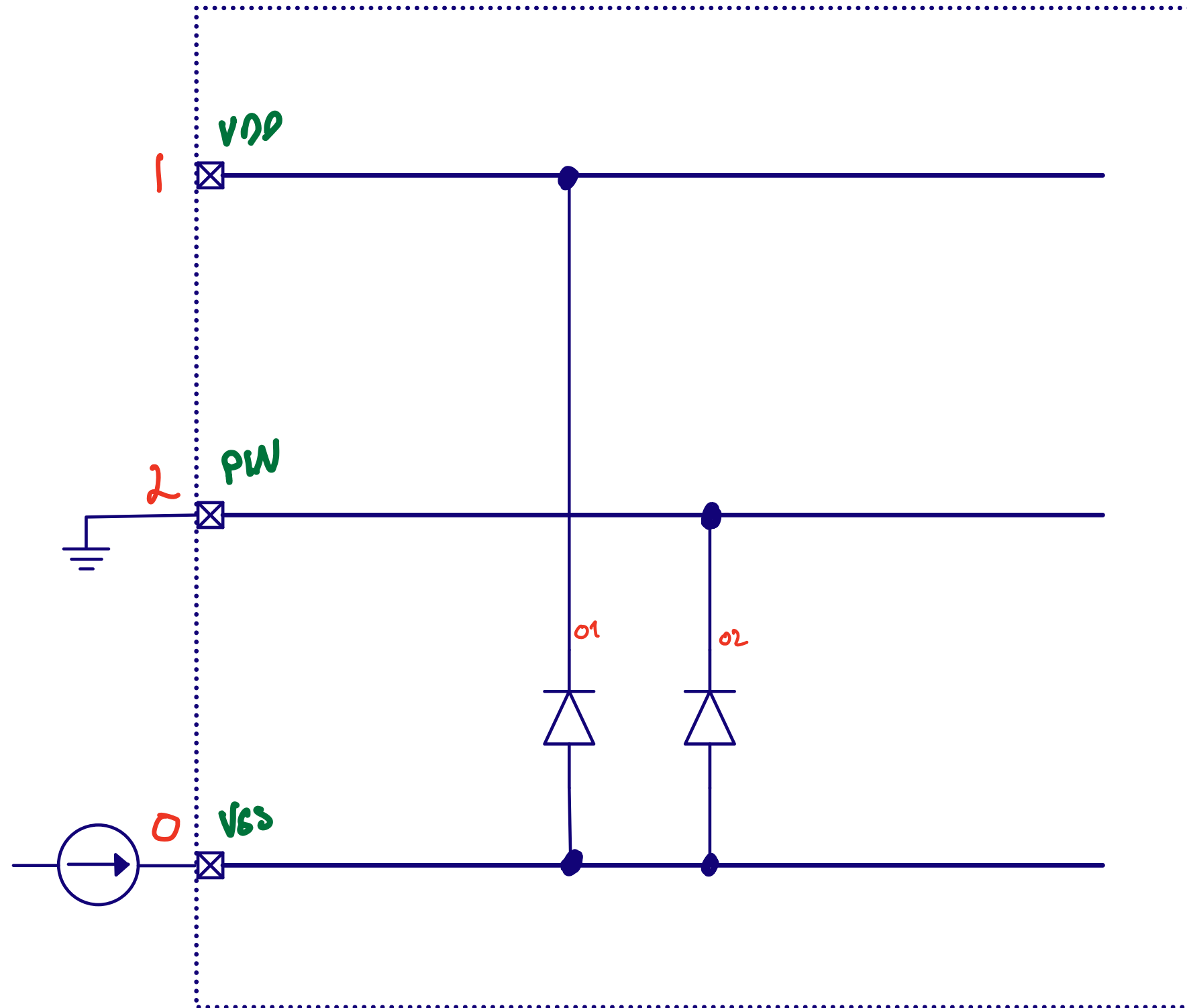

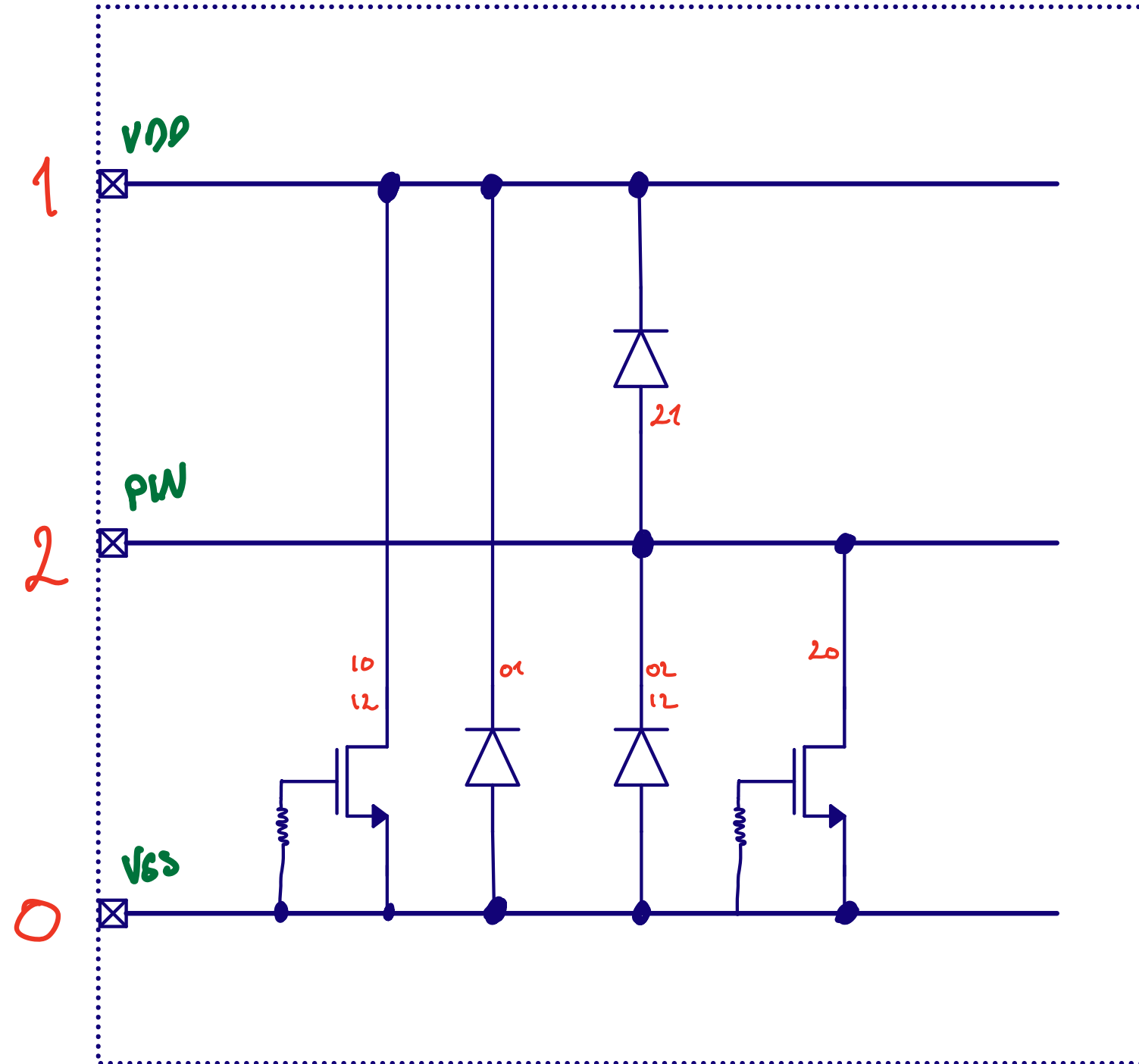~~0 → 1 = 01~~
~~1 → 0 = 10~~
~~0 → 2 = 02~~
~~2 → 0 = 20~~
~~1 → 2 = 12~~
~~2 → 1 = 21~~



 

Q: Why does this work?

If you don't do the layout right³

 


Fig. 5. Layout top view of the self-protecting fully silicided I/O buffer in a CMOS IC product.


 


Fig. 6. SEM image of the fully silicided I/O buffer without ballasting after 2-kV PS-mode ESD stress. ESD failure is found on only one finger of the driver NMOS. Current filamentation is also observed on the surface of the driver NMOS without ballasting.

 ³ [New Ballasting Layout Schemes to Improve ESD Robustness of I/O Buffers in Fully Silicided CMOS Process](#)



Q: How can current in one place lead to a current somewhere else?

You must **always handle ESD** on an IC

- Do everything yourself
- Use libraries from foundry
- Get help www.sofics.com

Thanks!